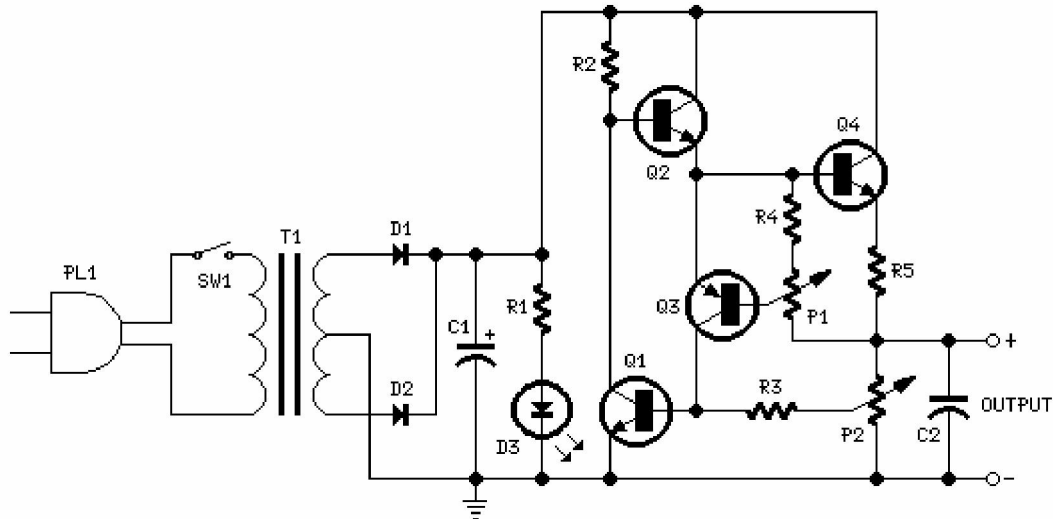


Variable DC Power Supply

Voltage range: 0.7 - 24V
Current limiting range: 50mA - 2A



Parts:

P1	_____ 500R	Linear Potentiometer
P2	_____ 10K	Log. Potentiometer
R1,R2	_____ 2K2	1/2W Resistors
R3	_____ 330R	1/4W Resistor
R4	_____ 150R	1/4W Resistor
R5	_____ 1R	5W Resistor
C1	_____ 3300 μ F	35V Electrolytic Capacitor (see Notes)
C2	_____ 1 μ F	63V Polyester Capacitor
D1,D2	_____ 1N5402	200V 3A Diodes
D3	_____ 5mm.	Red LED
Q1	_____ BC182	50V 100mA NPN Transistor
Q2	_____ BD139	80V 1.5A NPN Transistor
Q3	_____ BC212	50V 100mA PNP Transistor
Q4	_____ 2N3055	60V 15A NPN Transistor
T1	_____ 220V Primary, 36V Center-tapped Secondary	50VA Mains transformer (see Notes)

Device purpose:

A Variable DC Power Supply is one of the most useful tools on the electronics hobbyist's workbench. This circuit is not an absolute novelty, but it is simple, reliable, "rugged" and short-proof, featuring variable voltage up to 24V and variable current limiting up to 2A. Well suited to supply the circuits shown in this website. You can adapt it to your own requirements as explained in the notes below.

Notes:

P1 sets the maximum output current you want to be delivered by the power supply at a given output voltage.

P2 sets the output voltage and must be a logarithmic taper type, in order to obtain a more linear scale voltage indication.

You can choose the Transformer on the grounds of maximum voltage and current output needed.

Best choices are: 36, 40 or 48V center-tapped and 50, 75, 80 or 100VA.

Capacitor C1 can be 2200 to 6800 μ F, 35 to 50V.

Q4 must be mounted on a good heatsink in order to withstand sustained output short-circuit.

In some cases the rear panel of the metal box in which you will enclose the circuit can do the job.

The 2N3055 transistor (Q4) can be replaced with the slightly less powerful TIP3055 type.

Excellent quality-price ratio: enjoy!